

CS M151B:
Computer Systems Architecture
Week 3

Adder Progress

- Ripple Carry Adder:
 - Too slow, 160T delay for last result (Cout₃₁) based fan-out metric.
 - Problem: Each adder relies on the computation of previous adder's Cout
- Pure Carry Lookahead Adder:
 - Redundant calculations based on signals that are ready at time 0.
 - Better performance: 68T delay for last result.
 - Problem: Too large/impractical, fan-out of 32 (!)

Adder Progress

- Partial Carry Lookahead:
 - Create small CLA modules and chain them together, ripple style.
 - Better use of space, slower than full Carry Lookahead based on the current metric used (fan-in of $n \Rightarrow n \cdot T$ delay).
- Can we do better?
 - Like, waaay waaay better?

Hierarchical CLA

- Notice that each CLA unit consists of a C_{in} , two 4-bit inputs, and a C_{out} .
- This is like a 4-bit full adder!
- When combine via ripple style, each CLA unit must wait for previous CLA's C_{out} , which causes a delay.
- Let's combine these CLA units in CLA style.
- Why does this help?

Terminology

- C_n = Cin to unit n
- S_n = Sum out of unit n
- G_n = Generate of unit n (G_a , G_b , etc.)
- P_n = Propagate of unit n
- Delay of gate with fan-in of n is $n \cdot T$ (this is not always true!)

Note

- The following slides are to be used in conjunction with the lecture 3 slides, pg. 23-28.

Hierarchical CLA

- Recall that the S_3 and C_4 of a 4-bit CLA unit has delay $12T$.
- We don't want to wait that long for the second CLA unit to be ready.
- We would like the C_{in} to each CLA unit to be based on C_0 rather than C_4 , C_8 , C_{12} , etc.

Hierarchical CLA

- We do this by creating a Propagate and Generate signal for each CLA unit.
- $G_a = G_0 * P_1 * P_2 * P_3 + G_1 * P_2 * P_3 + G_2 * P_3 + G_3$
- $P_a = P_0 * P_1 * P_2 * P_3$
- The time for each G_x is 10T and the time for each P_x is 6.
- $C_4 = G_a + C_0 * P_a$
 - C_4 ready at 12T. This isn't any different from before.

Hierarchical CLA

- $C8 = Gb + Ga * Pb + C0 * Pa * Pb$
 - C8 ready at 15T. This IS different.
- $C12 = Gc + Gb * Pc + Ga * Pb * Pc + C0 * Pa * Pb * Pc$
 - C12 ready at 17T
- ...and so on.
- C32 (or cout_31) is 27 T (!)
- Is this the max latency from this module?

Hierarchical CLA

- No, we still need S31, which is still defined by:
 $S31 = (A31 \wedge B31) \wedge C31$, but remember that this is also a CLA module which means that C31 is actually created as $C31 = G30 + G29 * P30 + \dots + C28 * P28 * P29 * P30$
- C28 is ready at 25T
- C31 is ready at 33T
- S31 is ready at 35T
- This is a very good result, but this will require 8 CLA units together, which means the last values will require fan-in of 8.

Hierarchical CLA

- Let's add one last abstraction
- Rather than:
 - A single level-two hierarchical CLA with 8 level-one CLAs,
- Let's have:
 - Two level-two hierarchical CLA's with 4 level-one CLAs, chained together ripple style.

Hierarchical + Ripple CLA

- Out of first hierarchical CLA, C16 is 19T.
- Now from second hierarchical CLA, Cin is 19T.
- $C20 = Ga + C16 * Pa$
- Etc..
- Note that with the previous Full Hierarchical, the latency came from the term $Ga * Pd * Pc * Pb$ rather than $C0 * Pd * Pc * Pb * Pa$
- $C32 = 29T$
- What about S31?

Hierarchical + Ripple CLA

- $S_{31} = (A_{31} \wedge B_{31}) \wedge C_{31}$
- $C_{31} = G_{30} + G_{29} * P_{30} + \dots + C_{28} * P_{28} * P_{29} * P_{30}$
- Except now, C_{28} is 27T
- $S_{31} = 37T$
- Recall that the original Ripple Carry was around 160T and even the full CLA was around 65T. Be amazed!
- Had enough yet?

No you haven't

- Let's take a step back. The Ripple Carry adder would still be the most convenient if not for the fact that you had to cascade carries.
- Ideally, we want all results to be completed simultaneously, but this is impossible.
- However, perhaps all of the calculations can be done simultaneously.

Carry Select Adder

- Let's make a Ripple Carry Adder, except instead of waiting for the previous adder's carry to be done to use it, for each adder, do both calculations as if carry in is 0 or 1.
- This requires two adders per bit.
- Now, once the carry out is calculated, simply tell the next unit which results to use.
- $C_{out} = (A \& B) \mid (B \& C_{in}) \mid (A \& C_{in})$
- $S = (A \wedge B) \wedge C_{in}$

Carry Select Adder

- $C_{out} = (A \& B) \mid (B \& C_{in}) \mid (A \& C_{in})$
- $S = (A \wedge B) \wedge C_{in}$
- C_{out} is ready in $5T$
- S is ready in $4T$
- Each adder has the possible results ready in this time. The C_{out} must simply propagate to tell all of the other units.
- Each propagation now only adds cost of choosing which result to use (muxing)

Carry Select Adder

- C1 is ready in $5T$
- S0 is ready in $4T$
- C2 is ready in $5T + M$
- S1 is ready in $4T + M$
- C3 is ready in $5T + 2M$
- ...
- C32 is ready in $5T + 31M$
- S31 is ready in $4T + 31M$

Carry Select Adder

- M is probably pretty small, but having 31 M's is going to add up.
- We turn to our good friend the CLA
- Instead, chain eight, 4-bit CLA's with the same concept of doubling up on calculations.

Carry Select Adder

- C4 in 4-bit CLA is $12T$
- S3 in 4-bit CLA is $12T$
- C8 is ready in $12T + M$
- S7 is ready in $12T + M$
- ...
- C32 is ready in $12T + 7M$
- S31 is ready in $12T + 7M$
- Are we done yet?

Tradeoffs

- What were the tradeoffs that have driven this process?

Tradeoffs

- What were the tradeoffs that have driven this process?
 - Time
 - Space (fan-out)
 - Space (redundant gates to do redundant computation)

Tradeoffs

- The Ripple Carry was the smallest and simplest, but slowest.
- How did full CLA improve upon the Ripple Carry?

Tradeoffs

- The Ripple Carry was the smallest and simplest, but slowest.
- How did full CLA improve upon the Ripple Carry?
 - Redundant operations to deal strictly with inputs that were ready at time 0.
- How did the Partial Carry improve upon or worsen compared to full CLA?

Tradeoffs

- How did the Partial Carry improve upon or worsen compared to full CLA?
 - Full CLA had very wide, operations with very low depth. ($P_{31} * P_{30} * P_{29} * \dots * G_0$)
 - Reduce the width of operations but increase the depth. Ultimately more operations and a bit slower.
Note: This may not be true in the real world as a gate with a fan-in of 32 may actually incur a very significant delay.
- How did the single Hierarchical CLA improve upon the Full and Partial CLA?

Tradeoffs

- How did the Hierarchical CLA improve upon the Full CLA?
 - Add even more redundant computations, doing computations in different order.
- How did the Carry Select improve (depending on MUX time) upon the Hierarchical CLA?

Tradeoffs

- How did the Carry Select improve (depending on MUX time) upon the Hierarchical CLA?
 - Full redundancy with respect to the one unpredictable factor (carry in). Doubled all of the hardware.
- How do we improve upon Carry Select?

Midterm Review: Performance

- $ET = CPI * IC * CT$
- Assume for a given processor the following stats:

	Arith	Load/Store	Branch
Cycles	1	10	3
No. Insns	$500 * 10^6$	$300 * 10^6$	$100 * 10^6$

Midterm Review: Performance

- Suppose we find a way to double the performance of arithmetic instructions. What is the overall speedup of our machine? What if we find a way to improve the performance of arithmetic instructions by 10 times?

Midterm Review: Performance

- Old:
 - $IC = 900 * 10^6$
 - $CPI = 5/9 * 1 + 3/9 * 10 + 1/9 * 3 = 38/9$
 - $ET_o = 38/9 * 900 * 10^6 * CT = 3800 * 10^6 * CT$
- Improve arith by 2:
 - $IC = \text{SAME}$
 - $CPI = 5/9 * \frac{1}{2} + 3/9 * 10 + 1/9 * 3 = 71/18$
 - $ET_n = 3550 * 10^6 * CT$
- “Speedup”?

Midterm Review: Performance

- Old:
 - $ET_o = 3800 * 10^6 * CT$
- Double:
 - $ET_n = 3550 * 10^6 * CT$
- What percent did we reduce original time by?
- How many times faster is the new time?

Midterm Review: Performance

- Old:
 - $ET_o = 3800 * 10^6 * CT$
- Double:
 - $ET_n = 3550 * 10^6 * CT$
- What percent did we reduce original time by?
 - $ET_o * (1 - n) = ET_n$
 - $n = .0658$
- How many times faster is ET_n ?
 - $ET_o/ET_n = 1.0704$

Midterm Review: Performance

- Old:
 - $ET_o = 3800 * 10^6 * CT$
- Improve arith by 10:
 - $ET_n = 3350 * 10^6 * CT$
- What percent did we reduce original time by?
 - $ET_o * (1 - n) = ET_n$
 - $n = .1184$
- How many times faster is ET_n ?
 - $ET_o/ET_n = 1.1343 \Rightarrow$ NOT MUCH BETTER, AMDAHL STRIKES AGAIN!

Midterm Review: Tradeoffs

- In general, what can affect CPI?

Midterm Review: Tradeoffs




- In general, what can affect CPI?
 - Change how the program is written to use different proportions of instruction types (recall CPI is average over entire program)
 - Change how the program is compiled to use different proportions blah blah blah.
 - The types of instructions that the ISA defines: more complicated ones may mean more CPI and simpler ones may mean fewer CPI.

Midterm Review: Tradeoffs

- In general, what can affect CPI?
 - Change the complexity of hardware (ie adding/removing/splitting modules)


Midterm Review: Tradeoffs

- Add module:

   

Midterm Review: Tradeoffs


- Split module:

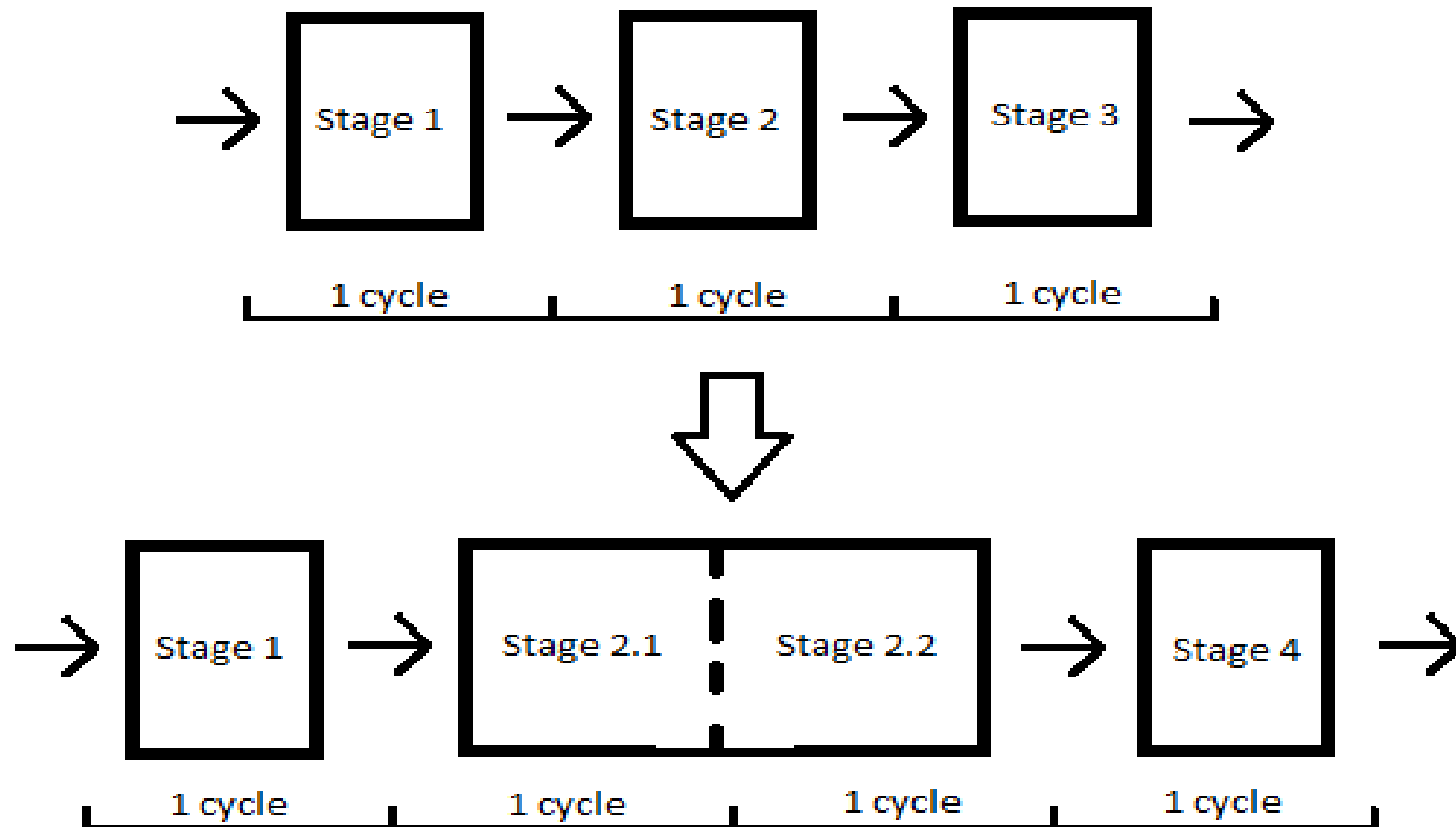

- Why might we do this?
- Could we add a module but decrease CPI?

Midterm Review Tradeoffs

- Sure:

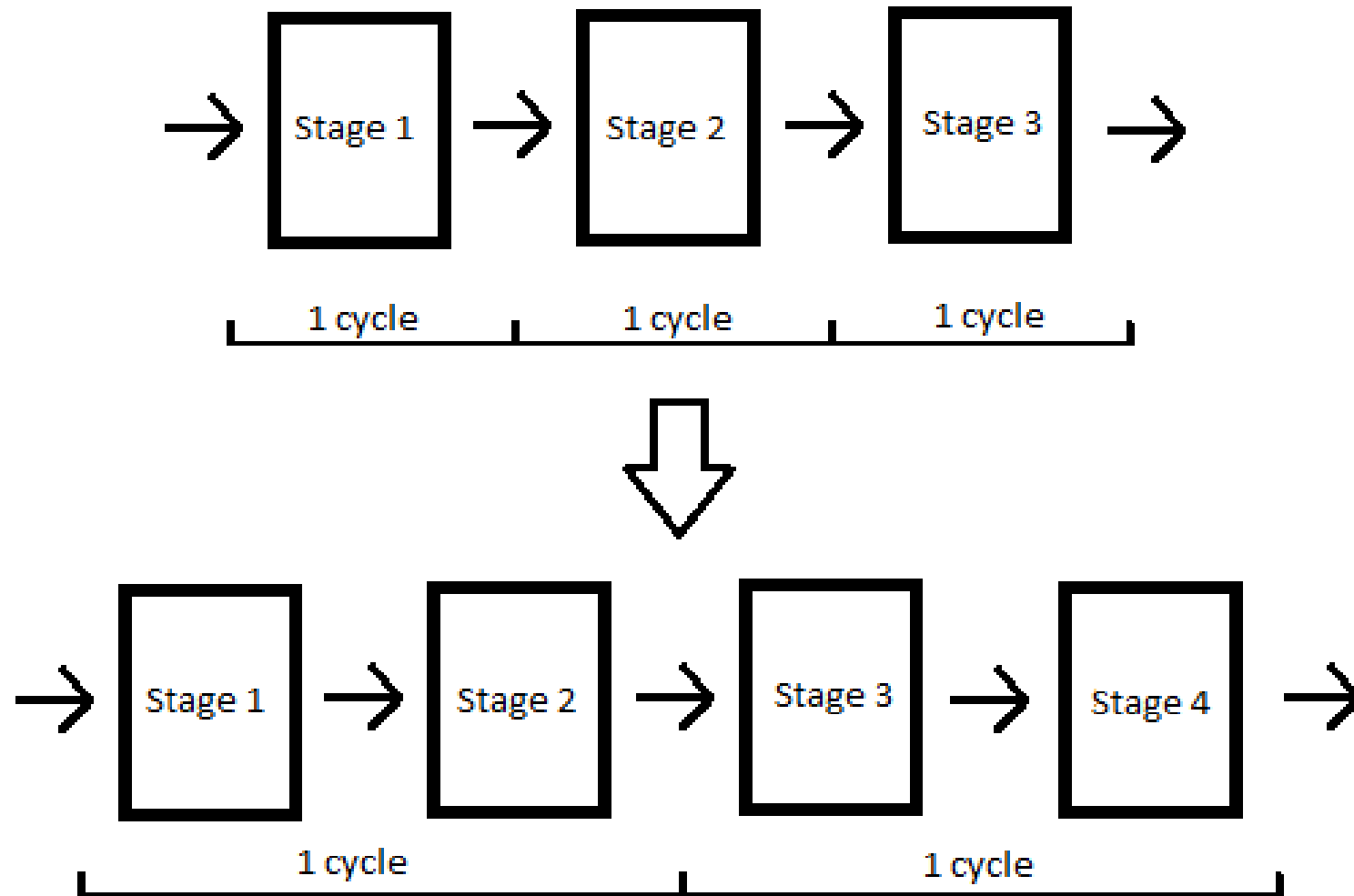

- What else have we changed now?

Midterm Review: Tradeoffs

- In general, what can affect CT?

Midterm Review: Tradeoffs

- In general, what can affect CT?
 - Mostly microarchitecture stuff.
 - Change CT so that multiple modules are expected to complete in one clock cycle.
 - Split a one cycle module into two modules, each of which takes one cycle.
 - Will splitting always change the clock time?

Midterm Review: Tradeoffs

- Will splitting always decrease the clock time?
 - No. If original module was the bottleneck, then the CT will decrease.
 - However, if the original module was not the bottleneck, then the CT cannot be changed since the bottleneck lies elsewhere and there is still a module that expects to complete in one clock cycle.

Midterm Review: Tradeoffs

- In general, what can affect IC?
 - Program written/compiled differently to choose more or fewer instructions.
 - The type of instructions that the ISA defines. If ISA defines many complex instructions IC may go down. If ISA defines only simple instructions, IC may go up.

Midterm Review: Tradeoffs

- An example mentioned in class:
- Consider J-Type instructions:
- [6 bits][26 bits]
- opcode addr
- What if we want to change it so that we only use 25 bits for addr. What affect could this have?

Midterm Review: Tradeoffs

- New format (assume fixed-length):
- [7 bits][25 bits]
- opcode addr
- What are the direct effects?

Midterm Review: Tradeoffs

- 6 bit opcode \rightarrow 7 bit opcode
- More operations:
 - 64 j-type instructions \rightarrow 128 j-type instructions
- 26 bit addr \rightarrow 25 bit addr
- Lower jump range:
 - $[PC + 4]_{31-28} : ADDR * 4 \rightarrow [PC + 4]_{31-27} : ADDR$
* 4
- What indirect effects could these direct effects have?

Midterm Review: Tradeoffs

- IC?

Midterm Review: Tradeoffs

- IC?
 - Increase: need to resort to direct jumping more often (load address into register, then use jr)
 - Decrease: more instructions to choose from, may simplify other operations

Midterm Review: Tradeoffs

- CPI?

Midterm Review: Tradeoffs

- CPI?
- Do the new instructions increase the complexity of the microarchitecture? If yes, then CPI may have increased.
- The cost of resorting to use `add + jr` instead may have changed proportion of instruction types, changing CPI.
- Using the new instructions could have changed the proportion of instruction types, changing CPI.

Midterm Review

- CT?

Midterm Review

- CT?
- In what way has the microarchitecture changed?
- If we split a bottleneck into two cycles, the CT may have decreased.
- If we simply make the a module more complex, we may increase the CT to accommodate.

End of
The Third Week

-Seven Weeks Remain-